


Advanced Task 1-2 RGB LED — Layering Three Inputs

Control an RGB LED with three inputs, each layering on top of the last

● R = Button (digital input)


● G = Serial input (from the Serial Monitor)

● B = Variable resistor (analog input)

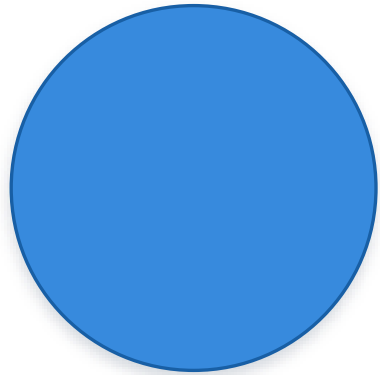

Variable resistor is dialed

Blue

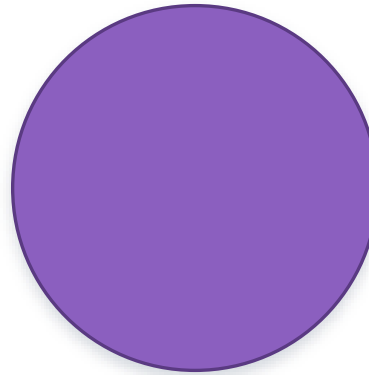

+ press button

Purple



+ serial input "1"

White




Hints

所有color pin都各需要接一個限流電阻!

- All of these are what we have done in basic tasks. Just combine them!
- When you get one color turned on, move on to the next.
- Connect the longest pin of the LED to the GND pin of the Arduino board.

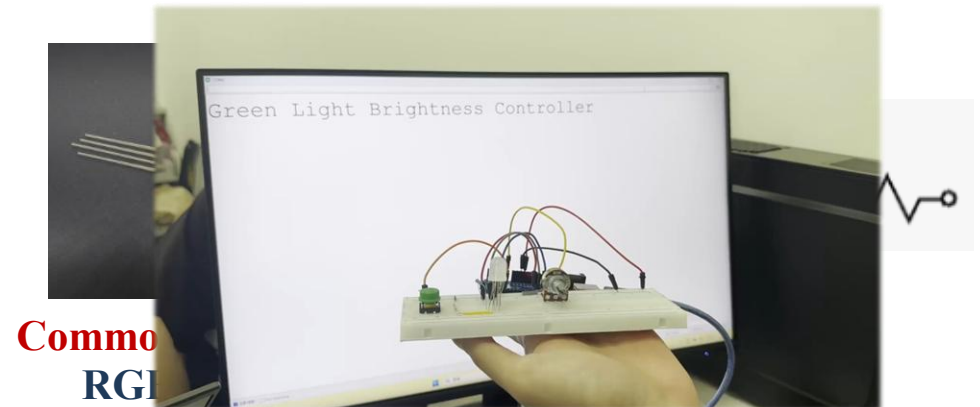The current limiting resistors are required for all color pins of the LED.



Common
RGB