

Advanced Task 2-1 Potentiometer Direction & Speed Control


🎯 Demo goal

Add a variable resistor to the previous circuit, and use its angle to control both the motor's direction and speed.

Increased counterclockwise
rotation speed

Increased clockwise
rotation speed

Stop

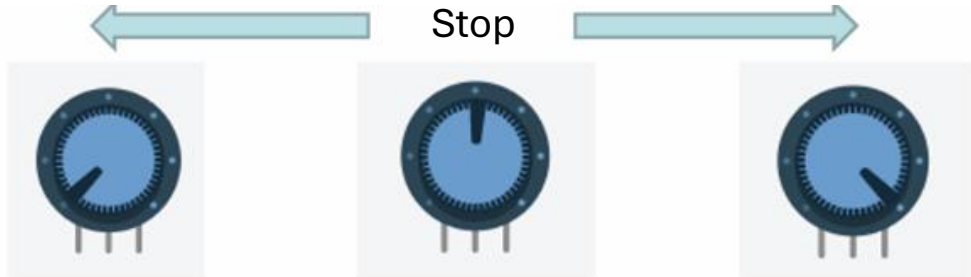

Variable resistor

